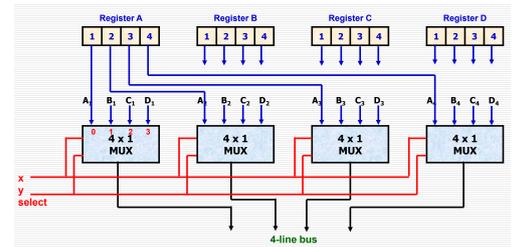


## Assignment 1

[3] A digital computer has a common bus system for 16 registers of 32 bits each. The bus is constructed with multiplexers.

- How many selection inputs are there in each multiplexer?
- What size of multiplexers are needed?
- How many multiplexers are there in the bus?

- Selection input number of each multiplexer =  $\log_2[\text{number of registers}]$
- Size of each multiplexer = number of registers
- Number of multiplexer = size of each register



Solution

# number of registers  $N = 16$  registers

# size of each register  $n = 32$  bits

(a) number of selection input =  $\log_2 16 = 4$

(b) size of each multiplexer = 16

(c) number of multiplexer = 32

Eng. Emad Mahdy **si** الكورسات كاملة علي موقع  
 +20 12 7148 2006

[www.si-manual.com](http://www.si-manual.com)

<https://www.youtube.com/@eng.emadmahdy>

<https://si-manual.com/courses/computer-architecture/>