


Assignment 1

Eng. Emad Mahdy **si** الكورسات كاملة علي موقع
+20 12 7148 2006
www.si-manual.com

[5] Draw the block diagram for the hardware that implements the following statements:

$$x + yz: AR \leftarrow AR + BR$$

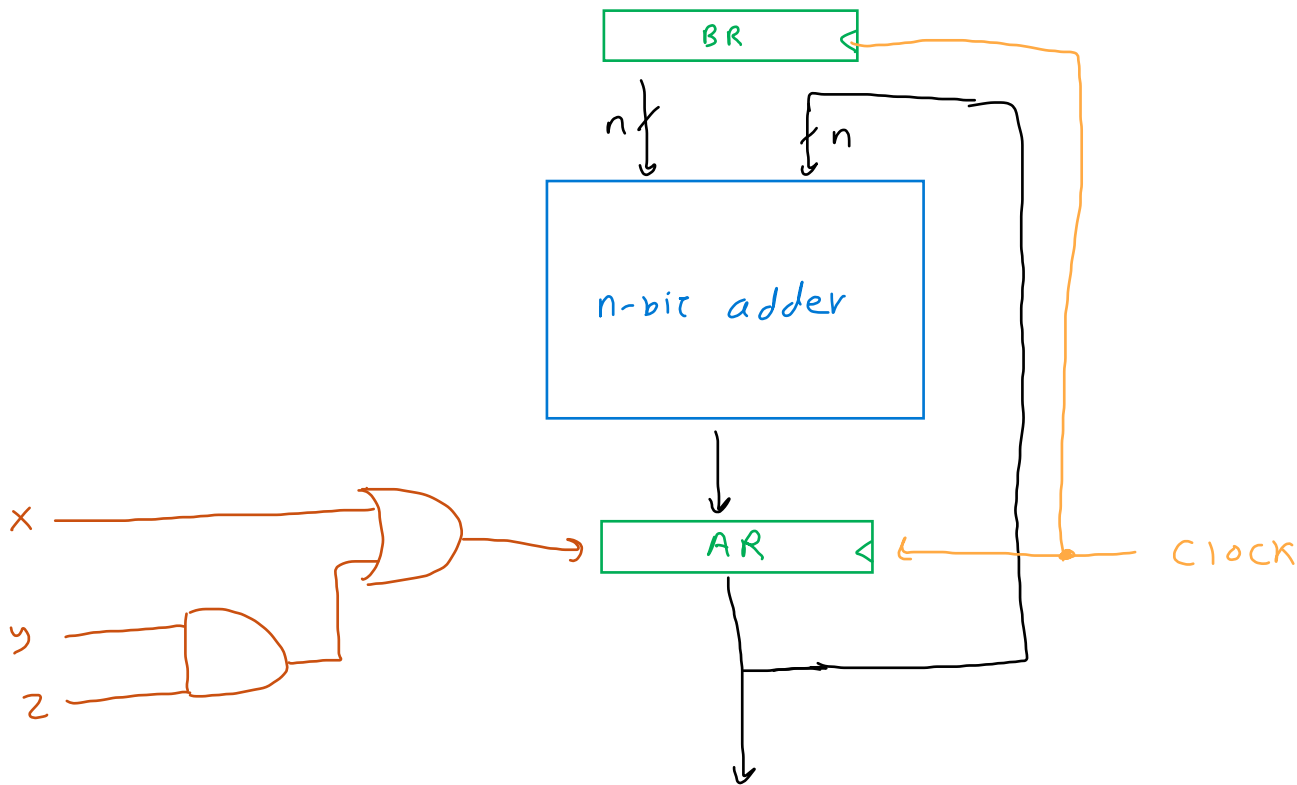where AR and BR are two n-bit registers and x, y, and z are control variables. Include the logic gates for the control function.



Eng. Emad Mahdy **si** الكورسات كاملة علي موقع
+20 12 7148 2006
www.si-manual.com

<https://www.youtube.com/@eng.emadmahdy>

<https://si-manual.com/courses/computer-architecture/>